

EES - Electrical & Electronics System

29/01/2025 - Lecture 1

Basic information about EES

30/01/2025 - Lecture 2

1) Electric circuit

- Interconnection of simple electrical devices with at least one closed path in which current may flow.
- An electric circuit is a mathematical model that approximates the behaviour of an actual electrical system.
- Consists of various elements
 - Resistor
 - Inductor
 - Capacitor
 - Voltage
- Circuit elements
 - 2 terminal components that cannot be sub-divided
 - Described mathematically in terms of its terminal voltage
- Basic circuit elements
 - Active Elements
 - Dependent Sources (*not in syllabus*)
 - Independent Sources
 - Voltage Sources
 - Ideal DC Voltage Source
 - Practical DC Voltage Source
 - Current Sources
 - Ideal DC Current Source
 - Practical DC Current Source
 - Passive Elements
 - Resistors
 - Inductors
 - Capacitors

2) Ohm's Law

To apply Ohm's law we must pay careful attention to the direction of current, the direction of current i and voltage v must conform with passive sign convention

If current is flowing from lower polarity to higher polarity then $v = -ir$

- Value of R , R can range from $0 \rightarrow \infty$
 - An element with $R = 0$ is called a short circuit, $v = ir = 0$
- If R is infinity then it is called an open circuit
 - For an open circuit, $i = v/r = 0$
 - Voltage may be having some value but current will be zero
- Not all resistors obey Ohm's law, the resistors which obey Ohm's law are known as Linear Resistor

3) Sources

- Ideal Nature
 - Ideal voltage source maintains a prescribed voltage regardless of current in device, Internal Resistance = 0
 - An ideal current source maintains prescribed current regardless of the voltage

4) Source transformation

- Conversion of practical voltage source to the Current Source and vice versa
 - Voltage & Current sources shown in figure are electrically equivalent

